

Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

*Do NOT begin until told to do so*  
*Make sure that you have all pages before starting*  
*You may not leave the room during the exam*  
*No calculators, open book, open notes*

## ACADEMIC INTEGRITY:

Students have the responsibility to know and observe the requirements of The UNCC Code of Student Academic Integrity (1997-99 Catalog page 336). This code forbids cheating, fabrication or falsification of information, multiple submission of academic work, plagiarism, abuse of academic materials, and complicity in academic dishonesty.

Useful constants, etc:

$$\begin{array}{cccc}
 e \approx 2.72 & \pi \approx 3.14 & 1/e \approx 0.37 & \sqrt{2} \approx 1.41 \\
 \sqrt{3} \approx 1.73 & \sqrt{5} \approx 2.22 & \sqrt{7} \approx 2.64 & \sqrt{10} \approx 3.16 \\
 \ln[2] \approx 0.69 & \ln[4] \approx 1.38 & \ln[55] \approx 4.0 & \ln[256] \approx 5.6 \\
 \log_{10}[2] \approx 0.30 & \log_{10}[3] \approx 0.48 & \log_{10}[55] \approx 4.0 & \log_{10}[10] \approx 1.0 \\
 \log_{10}[0.1] \approx -1.0 & \log_{10}[0.5] \approx -0.3 & \log_{10}[e] \approx 0.43 & \cos(\pi/4) \approx 0.79
 \end{array} \tag{1}$$


$$\cos(A)\cos(B) = \frac{1}{2}\cos(A - B) + \frac{1}{2}\cos(A + B)$$

$$e^{j\theta} = \cos(\theta) + j\sin(\theta)$$

$$\cos^2(A) = \frac{1}{2} + \frac{1}{2}\cos(2A)$$

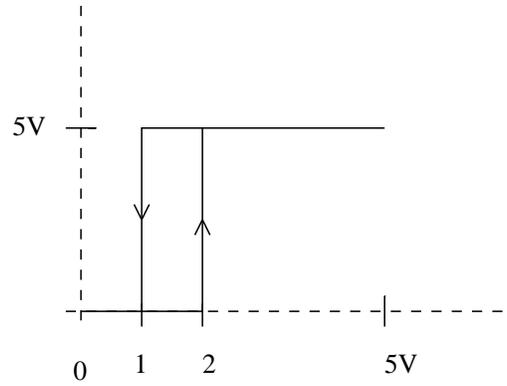1. 20 points

Design a bistable circuit for the following transfer function. Assume that the parts available to you are 0.1K to 1K resistors, 1 pF capacitors, and ideal op-amps. Assume the power supply is 5V. Show your design formulae, and show the final schematic.



2. 20 points

Design a 2 bit Flash analog-to-digital converter showing a schematic and any design calculations. For the output logic circuitry, do *not* draw a gate-level schematic, rather, draw a logic truth table. Assume that the parts available to you are 0.1K to 1K resistors, 1 pF capacitors, and ideal op-amps. Assume the power supply is 5V.

3. 20 points

A simple RC filter (series R, shunt C) is to be designed using a switched capacitor for the series resistor. Draw the schematic of the circuit. Assume that the parts available to you are 1 pF capacitors, and ideal switches. Design the series resistor for  $R = 1 \text{ MegOhm}$  and let the shunt capacitor be 10 pF.

4. 20 points


A 3-bit R2R DAC is constructed with  $R = 1\text{K}$  and a power supply of  $5\text{V}$ . Draw a schematic of the DAC assuming ideal op-amps and ideal switches.

5. 20 points

Below:

NMOS devices:  $K_p = 0.1A/V^2$ ,  $V_t = 1V$ ,  $W/L = 1$ ,  $\lambda = 0$

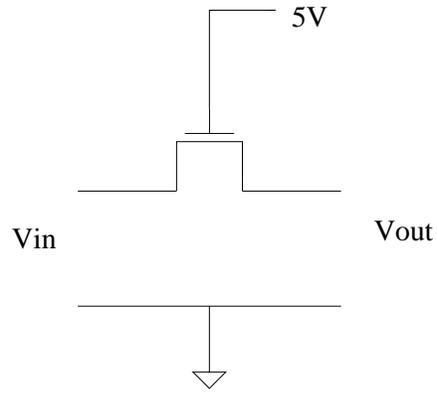a) Find the on-resistance and off-resistance of the NMOS switch below.



b) What is the maximum current that the switch can deliver to the output? Assume that the output is short-circuited and the input voltage remains between 0 and 5 Volts.