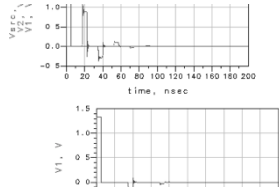


### Waves and Reflection, Pulses


- In high speed systems, you may have observed multiple reflections of pulses on circuit boards



- Therefore, transmission lines, waves, reflections serve important role in RF/microwave systems
- Optics and reflections are a great analogy

19

### Transmission Lines

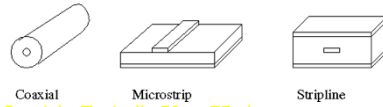


- Coaxial - Typically 50 or 75 ohms
- Twin-lead UHF - typ 300 ohms
- Microstrip
- Stripline
- Waveguide
- Coplanar waveguide
- Slot line


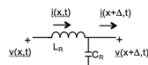
### Waves, LC Transmission Line

Orfanidis 10.6

- Why transmission lines at high frequency:
  - Finite velocity, time delay, and **waves!**
  - A ground wire may be an open circuit!



Lossless LC line relations:

$$\frac{\partial v(x,t)}{\partial x} = -L_n \frac{\partial i(x,t)}{\partial t} \Rightarrow \nabla \times E = -\mu \frac{\partial H}{\partial t}$$

$$\frac{\partial i(x,t)}{\partial x} = -C_n \frac{\partial v(x,t)}{\partial t} \Rightarrow \nabla \times H = \epsilon \frac{\partial E}{\partial t}$$

**Note:**  $k$  is wavenumber, or spatial frequency, and when purely real has units of radians/meter

$$v(x,t) = v_+(x,t) + v_-(x,t)$$

$$= \text{Re}\{V_+ e^{-jkz} e^{j\omega t} + V_- e^{jkz} e^{j\omega t}\}$$

$$v_+(x,t) = \text{Re}\{V_0 e^{-jkz} e^{j\omega t}\} = \text{Re}\{V_0 e^{-\gamma z} e^{j\omega t}\} = \text{Re}\{V_0 e^{-(\alpha + j\beta)z} e^{j\omega t}\}$$

Phasor notation drops  $e^{j\omega t}$ :  $E_0 e^{-\gamma z} e^{j\omega t}$  becomes  $E_0 e^{-\gamma z}$

$$\text{and } \nabla \times H = J + \epsilon \partial E / \partial t \Rightarrow \nabla \times H = J + j\omega \epsilon E \text{ with } E = E_0 e^{-\gamma z} e^{j\omega t}$$

Finally propagation constant  $\gamma = \alpha + j\beta$  and phase velocity  $v_p$

$$\gamma = j\omega / v_p = j\omega \sqrt{L_n C_n}, \text{ so wavelength } \lambda = v_p / f = 2\pi / \beta$$

$$\text{and characteristic impedance } Z_0 = v_+(x,t) / i_+(x,t) = \sqrt{L / C}$$

### Beware of Literature

- It is common in engineering literature to solve circuit equations, maxwell equations, and transmission line equations using phasors of the form  $\exp(j\omega t)$ :

$$\text{Phasor notation with } e^{j\omega t}: E_0 e^{-\gamma z} e^{j\omega t} \text{ becomes phasor } E_0 e^{-\gamma z}$$

$$\text{and } \nabla \times H = J + \epsilon \partial E / \partial t \Rightarrow \nabla \times H = J + j\omega \epsilon E$$

- Beware of physics/optics literature (use of  $i$  vs  $j$  **may** forewarn) solves maxwell equations and transmission line equations using phasors of the form  $\exp(-i\omega t)$ :

$$\text{Phasor notation with } e^{-i\omega t}: E_0 e^{jkz} e^{-i\omega t} \text{ becomes phasor } E_0 e^{jkz}$$

$$\text{and } \nabla \times H = J + \epsilon \partial E / \partial t \Rightarrow \nabla \times H = J + -i\omega \epsilon E$$

whereas an engineering text may use  $E_0 e^{-jkz} e^{j\omega t}$

**Note:** Yariv of Cal Tech is © 2001-2015 T.Weldon  
In the engineering camp

### Traveling Wave


Orfanidis 3.5

- Phase velocity

Time  $t=0, \theta=0, \alpha=0$   
 $\text{Re}\{V_p e^{j(\omega t + \theta)} e^{\alpha z} e^{-\beta z}\}$   
 $= \cos(\omega t - \beta z)$   
 $= \cos(-\beta z)$

Time  $t=\Delta t, \theta=0, \alpha=0$   
 $\text{Re}\{V_p e^{j(\omega t + \theta)} e^{\alpha z} e^{-\beta z}\}$   
 $= \cos(\omega \Delta t - \beta z)$   
 $= \cos(\omega \Delta t - \beta z)$

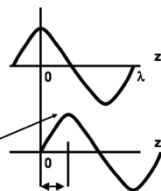Peak is where  $0 = \omega \Delta t - \beta \Delta z$   
 So  $\omega \Delta t = \beta \Delta z$  and  $\Delta z = \omega \Delta t / \beta$   
 Then velocity  $= \Delta z / \Delta t = \omega / \beta$



© 2001-2015 T.Weldon

### Group Velocity

Orfanidis 3.5

- Group velocity is velocity of energy travel

group velocity  $v_g = d\omega / d\beta$  is velocity of energy packet

consider:  $\cos(a) + \cos(b) = 2 \cos((a-b)/2) \cos((a+b)/2)$

for  $\cos(\omega_1 t - \beta_1 x) + \cos(\omega_2 t - \beta_2 x) = 2 \cos((\Delta\omega t - \Delta\beta x)/2) \cos((\Sigma\omega t - \Sigma\beta x)/2)$

where  $\beta = \omega / v_p, \Delta\omega = \omega_1 - \omega_2, \text{ and } \Delta\beta = \beta_1 - \beta_2$

at  $t=0$ , the peak of the envelope is at  $x=0$ , at  $t=\Delta t$ , the peak moves to  $\Delta x$  where

$$(\Delta\omega \Delta t - \Delta\beta \Delta x) / 2 = 0 \text{ so } \Delta x = \Delta\omega \Delta t / \Delta\beta$$

then, group velocity  $v_g$  is the envelope velocity

$$v_g = \lim_{\Delta t \rightarrow 0} \frac{\Delta x}{\Delta t} = \lim_{\Delta\omega \rightarrow 0} \frac{\Delta\omega}{\Delta\beta} = \frac{d\omega}{d\beta}$$

For the lossless LC line


$$v_p = \omega / \beta = 1 / \sqrt{L_n C_n}$$

so,  $\omega = \beta / \sqrt{L_n C_n}$ , then

$$v_g = \frac{d\omega}{d\beta} = 1 / \sqrt{L_n C_n} = v_p$$

**Note:**  $v_g$  does not always equal  $v_p$

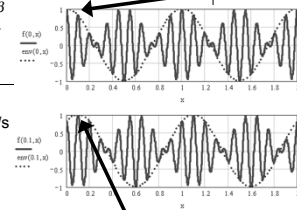Example:  
 $v_g = v_p = 1 \text{ m/s}$   
 $f_1 = 11 \text{ Hz}$   
 $f_2 = 9 \text{ Hz}$



At  $t=0.1$ , peak at  $x=0.1$

© 2001-2015 T.Weldon

### Lossy Line Orfanidis 10.6

- Include resistance R (ohm/m) in series with L (H/m)
- Include conductance G (S/m) in parallel with C (F/m)

Lossy RLGC line propagation constant and phase velocity  $v_p$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

where  $V_0 e^{-\gamma s} e^{j\omega t} = V_0 e^{-(\alpha + j\beta)s} e^{j\omega t} = V_0 e^{-\alpha s} e^{-j\beta s} e^{j\omega t}$

and then  $\beta = \text{Im}\{\gamma\} = \text{Im}\{\sqrt{(R + j\omega L)(G + j\omega C)}\}$

so wavelength  $\lambda = v_p / f = 2\pi / \beta$

and phase velocity  $v_p = \omega / \beta$

and attenuation constant  $\alpha$  is

$$\alpha = \text{Re}\{\gamma\} = \text{Re}\{\sqrt{(R + j\omega L)(G + j\omega C)}\}$$

and characteristic impedance

$$Z_0 = \sqrt{(R + j\omega L) / (G + j\omega C)}$$

### Time Domain Reflections Orfanidis 10.15

See Ludwig Fig. 2-23, 2-24 and 2-34

**Source**  
 $2V_0, R_s \text{ or } Z_s$

Incident wave  $\rightarrow$

Reflected wave  $\leftarrow$

**LOAD**  
 $Z_L$

### Reflection Coefficient

- It is easiest to analyze wave phenomena using the reflection coefficient, gamma:

$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s}$$

where  $Z_L$  is source and  $Z_s$  is load impedance

Note: approach here may differ from some textbooks

At input interface, incident wave  $V_+ = V_s / 2$

At input interface, reflected wave  $V_- = \Gamma V_+$

At input interface, total voltage  $V_T = V_+ + V_- = (1 + \Gamma)V_s / 2 = \frac{Z_L V_s}{Z_L + Z_s}$

As a pulse makes multiple reflections, repeat the above process where the source impedance becomes the line impedance, and the load alternately becomes the generator and load

© 2001-2015 T.Weldon

### Simple Examples Without a Line

- Short circuit load

$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{0 - Z_s}{0 + Z_s} = -1$$

incident wave  $V_+ = V_s / 2$

reflected  $V_- = \Gamma V_+ = -V_+ = -V_s / 2$

total voltage:  
 $V_T = V_+ + V_- = (1 + \Gamma)V_s / 2 = 0$

As expected,  
**0 volts across the short circuit**

- Open circuit load

$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{\infty - Z_s}{\infty + Z_s} = 1$$

incident wave  $V_+ = V_s / 2$

reflected  $V_- = \Gamma V_+ = V_+ = V_s / 2$

total voltage:  
 $V_T = V_+ + V_- = (1 + \Gamma)V_s / 2 = V_s$

As expected,  
**all volts across the open circuit**

© 2001-2015 T.Weldon

### Simple Examples Without a Line

- Conjugate matched load

$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{Z_g^* - Z_g}{Z_g^* + Z_g} = \frac{-2j \text{Im}\{Z_g\}}{2 \text{Re}\{Z_g\}} = \frac{-j \text{Im}\{Z_g\}}{\text{Re}\{Z_g\}}$$

incident wave  $V_+ = V_s / 2$

reflected  $V_- = \Gamma V_+ = -V_+ = -V_s / 2$

total voltage:  
 $V_T = V_+ + V_- = (1 + \Gamma)V_s / 2 = \frac{(\text{Re}\{Z_g\} - j \text{Im}\{Z_g\})V_s}{2 \text{Re}\{Z_g\}} = \frac{Z_g^* V_s}{Z_g^* + Z_g}$

As expected,  
**the conjugate match voltage equals that of the voltage divider comprised of  $Z_g^*$  and  $Z_g$**

### Time Reflections in Lossless Line

Orfanidis 10.15 and See [http://thomasweldon.com/tpw/papers/aps2013\\_extraction\\_6jan13f\\_subppt.pdf](http://thomasweldon.com/tpw/papers/aps2013_extraction_6jan13f_subppt.pdf)

incident wave  $V_{s1} = V_s / 2$

$$\Gamma_1 = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{Z_0 - Z_s}{Z_0 + Z_s}$$

$$\Gamma_1 V_1 = \frac{Z_0 - Z_s}{Z_0 + Z_s} \frac{V_s}{2}$$

$$V_{s1} = V_{r1} = (1 + \Gamma_1) \frac{V_s}{2} = \frac{Z_0 V_s}{Z_0 + Z_s}$$

$$\Gamma_3 = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{Z_g - Z_0}{Z_s + Z_0} = -\Gamma_1$$

$$V_{s3} = (1 + \Gamma_3) V_{r2} = \Gamma_2 (1 - \Gamma_1^2) \frac{V_s}{2}$$

$$V_{s3} = \Gamma_2 V_{r2} = -\Gamma_1 \Gamma_2 (1 + \Gamma_1) \frac{V_s}{2}$$

incident  $V_{s1} = (1 + \Gamma_1) V_s / 2$

$$\Gamma_2 = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$V_{r2} = (1 + \Gamma_2) V_{s1} = (1 + \Gamma_2)(1 + \Gamma_1) \frac{V_s}{2}$$

$$V_{s2} = \Gamma_2 V_{s1} = \Gamma_2 (1 + \Gamma_1) \frac{V_s}{2}$$

incident  $V_{s3} = \Gamma_3 \Gamma_2 (1 + \Gamma_1) V_s / 2$

$$\Gamma_4 = \Gamma_3 = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$V_{r4} = -\Gamma_4 \Gamma_2 (1 + \Gamma_2)(1 + \Gamma_1) \frac{V_s}{2}$$


$$V_{s4} = \Gamma_4 V_{s3} = -\Gamma_1 \Gamma_2^2 (1 + \Gamma_1) \frac{V_s}{2}$$

etc.

© 2001-2015 T.Weldon
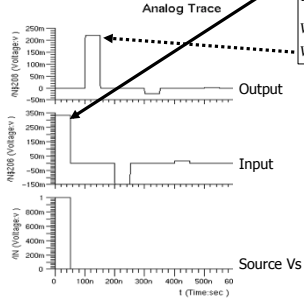
### Short Pulse Simulation

$R_s = 100$ ,  $Z_0 = 50$ ,  $R_L = 25$   
 Transmission line delay = 100 ns  
 Open-circuit source voltage  $V_s = 1$  V




$$\Gamma_1 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - R_s}{Z_0 + R_s} = \frac{50 - 100}{50 + 100} = -0.33$$

first reflection  $\Gamma_1 V_s = -0.33V_s / 2 = -0.165$   
 $V_{r1} = V_{r1} = (1 + \Gamma_1)V_s / 2 = (1 - 0.33)/2 = 0.33$

$$\Gamma_2 = \frac{Z_L - Z_s}{Z_L + Z_s} = \frac{R_L - Z_0}{R_L + Z_0} = \frac{25 - 50}{25 + 50} = -0.33$$

$$V_{r2} = \Gamma_2 V_{r1} = -0.33V_{r1} = -0.11$$
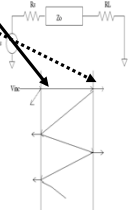
$$V_{r2} = (1 + \Gamma_1)V_{r1} = (1 + -0.33)(0.33) = 0.22$$



### Decibels

- Decibels, or dB, are  $10 \log_{10}$  (power ratio)  
 $10 \log_{10} (P / P_{ref})$
- Always power ratio!
- Typically relative to some reference  
 1V, 1W, milliwatt,  $\mu$ V
- Notation: dBx = dB relative to reference x
- dBm = dB relative to 1 milliwatt (Ludwig p. 491)
- Power in dBm units =  
 $10 \log_{10}$  (power in milliwatts / 1 milliwatt)
- Example: 0.0001 Watts =  
 $10 \log_{10} (0.1 \text{ mW} / 1 \text{ mW}) = -10 \text{ dBm}$

© 2001-2010 T.Weldon

### Decibels 2

- Power is proportional to voltage squared or current squared
- So translating a voltage ratio into power ratio requires square
- Factors of 2 in power=10dB, factors of 10 in power=10dB
- $\text{dB} = 10 \log_{10}$  (power ratio) =  
 $10 \log_{10} [V^2 / (V_{ref})^2] = 20 \log_{10} (V / V_{ref})$
- The 20 log comes from the square of the voltage
- Example: 10 V rms = 20 dBv
- What is 5 mW in dBm? In dBW?

© 2001-2010 T.Weldon

- Project 1

© 2001-2015 T.Weldon