

C MOS.
REVIEW



CHECK TEXTBOOK TO CORRECT
ANY ERRORS.

TWEEDON

REVIEW NOTES I

(1)

N-CHANNEL ENHANCEMENT MODE MOSFET

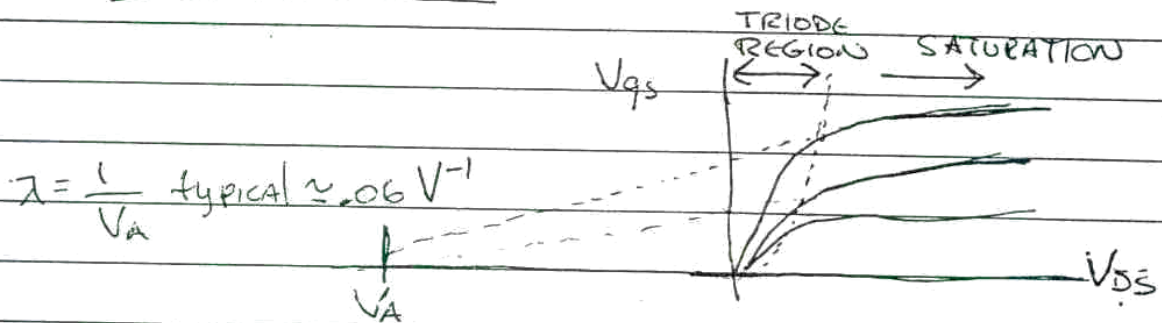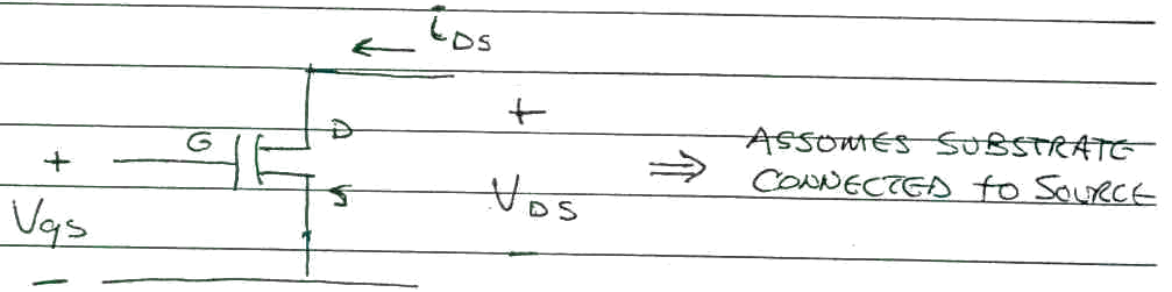

IN SATURATION REGION $V_{DS} \geq V_{GS} - V_T$

$$I_{DS} = \frac{W}{L} \frac{k_p}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

W, L = gate width & length, V_T = Threshold Voltage $\approx 0.8V$

$$k_p = \frac{\mu_n C_{ox}}{t_{ox}} = \frac{\mu_n \epsilon_{ox}}{t_{ox}} \approx \frac{4 \mu_n \epsilon_0}{t_{ox}} = \text{PROCESS TRANSCONDUCTANCE}$$

C_{ox} = CAPACITANCE/UNIT AREA, μ_n = Electron mobility
 t_{ox} = OXIDE THICKNESS, TYPICAL $k_p \approx 20 \mu A/V^2$

$$\text{Output Resistance} = \frac{1}{dI_{DS}/dV_{DS}} \approx \frac{1}{\lambda I_{DS}} = R_{DS}$$

Note: $\frac{k_p}{2}$ = MOSIS K' in process data

(λ = CHANNEL LENGTH MODULATION PARAM.)

(2)

In Triode Region. $V_{DS} < V_{GS} - V_T$


$$I_{DS} = k_p \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

here DRAIN = SOURCE BEHAVES LIKE A VOLTAGE VARIABLE RESISTOR where

$$R_{DS} = \frac{1}{k_p \frac{W}{L} (V_{GS} - V_T)}$$

Similarly

ENHANCEMENT MODE PFET

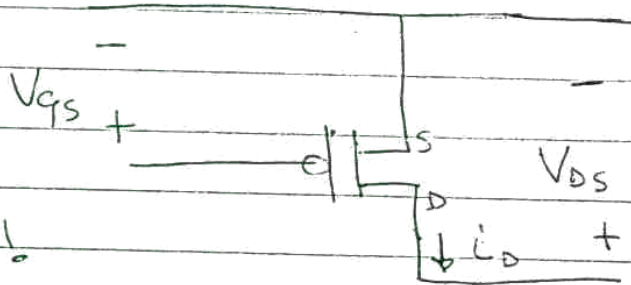

BOOK USES
DIFFERENT
CONVENTION!

Note: Different direction, i_D "out" of DRAIN
Also V_T AND V_{GS} ARE TYPICALLY NEGATIVE

$$I_D = \frac{W}{L} \frac{k_p}{2} (V_{GS} - V_T)^2 (1 + |\lambda V_{DS}|)$$


Body Effect

3

IF SOURCE IS NOT CONNECTED TO BULK

$$V_T = V_{T0} + \gamma \left(\sqrt{|2\phi_s| + V_{SB}} - \sqrt{|2\phi_s|} \right)$$

↑ NORMALLY POSITIVE FOR N-CHANNEL

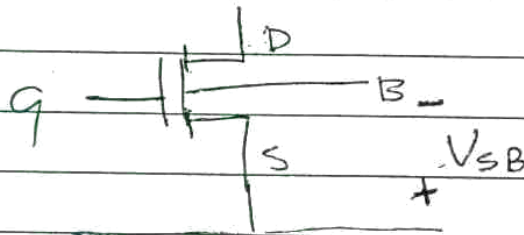

$$\phi_s \approx -0.3V$$

So V_T INCREASES AS V_{SB} INCREASES.

CONSIDER



U.S.




CAUTION THIS SINCE NO P-WELL

IN OUR PROCESS ALL NFETS BULK IS GROUND
SO! LEFT CASE HOLDS!

Small Signal Models

4

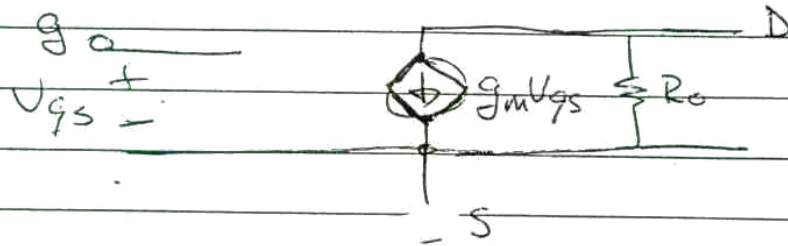

IN SATURATION

$$g_m = \frac{d i_D}{d v_{gs}} = \frac{\omega}{L} k_p (v_{gs} - V_T) (1 + \lambda v_{ds})$$

$$\approx \frac{\omega}{L} k_p (v_{gs} - V_T)$$

$$= \sqrt{2 \frac{\omega}{L} k_p i_D}$$

AND


$$R_o = \frac{1}{\lambda i_{Ds}} \quad \text{AS BEFORE.}$$

Another useful form, where $i_D \approx \frac{\omega}{L} \frac{k_p}{2} (v_{gs} - V_T)^2$

$$g_m \approx \frac{\omega}{L} k_p (v_{gs} - V_T) = \frac{2 i_D}{v_{gs} - V_T}$$



(5)

ADDING CAPACITANCES

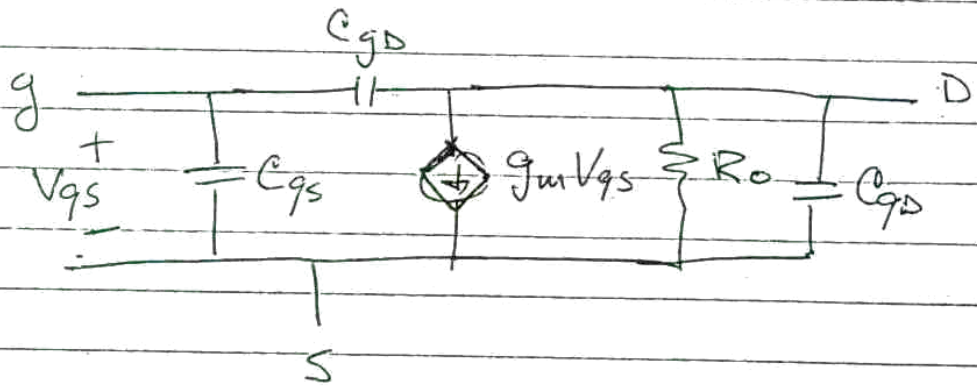

CONSIDER

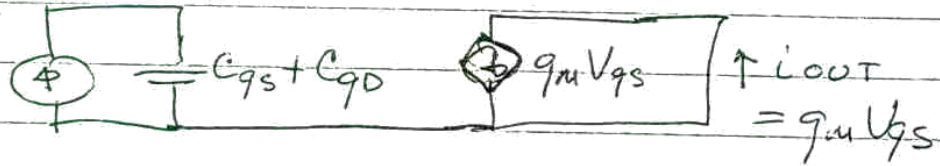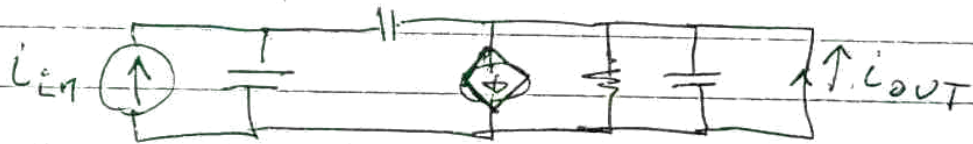- ① CURRENT SOURCE IN
- ② SHORT CIRCUIT OUT



$$\frac{i_{out}}{i_{in}} = \frac{g_m V_{gs}}{i_{in}} = \frac{g_m}{j\omega(C_{gs} + C_{gd})} = \frac{g_m}{\omega(C_{gs} + C_{gd})}$$


Unity Gain Frequency Figure of Merit

$$f_T = \frac{\omega_T}{2\pi} = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

CMOS Circuits

(6)

Current Mirror

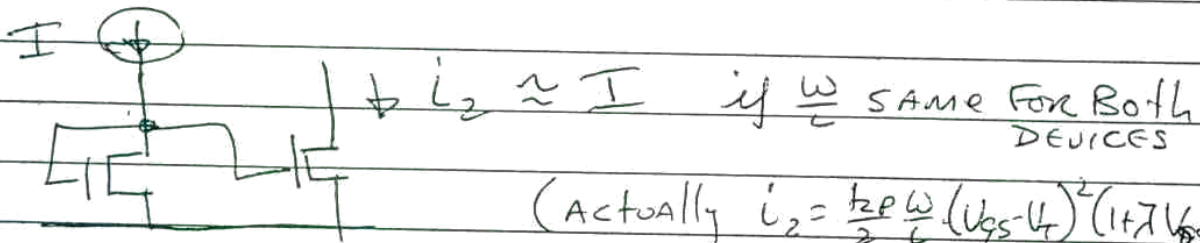

(ACTUALLY $i_2 = \frac{1}{2} \frac{\mu P W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$)



IN ABOVE, "minimum voltage"
OF USEFUL RANGE IS WHEN OUTPUT
FET IS IN SATURATION, I.E.


KEEP $V_{DS} \geq V_{GS} - V_T$ AT output

IN FIRST CASE ABOVE, note


$$R_o \approx \frac{1}{\lambda i_2}$$

OTHER CURRENT SOURCES!

(7)

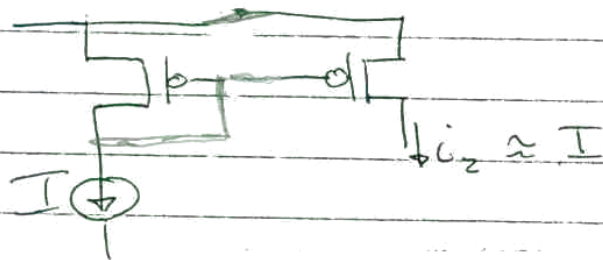

Example SIMPLIFIED ANALYSIS

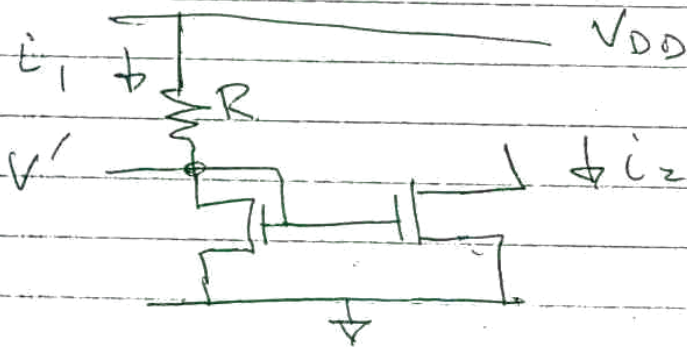


if R is very LARGE, $V' \approx V_T$

$$\text{So } i_1 \approx \frac{V_{DD} - V_T}{R} \approx i_2$$

Higher OUTPUT IMPEDANCE SOURCE


8

(Wilson Current Mirror)

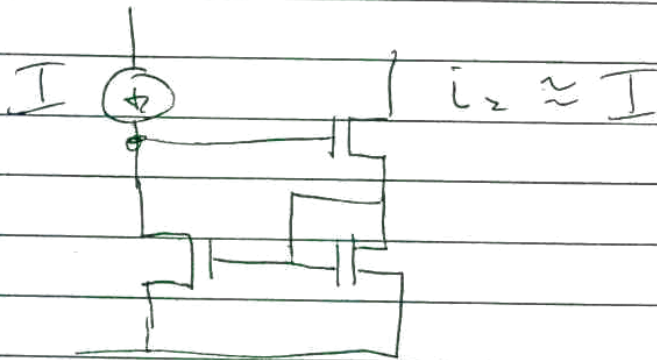

DISADVANTAGE: output voltage must be higher to bias 2 devices in output.


EVEN BETTER (MODIFIED WILSON)

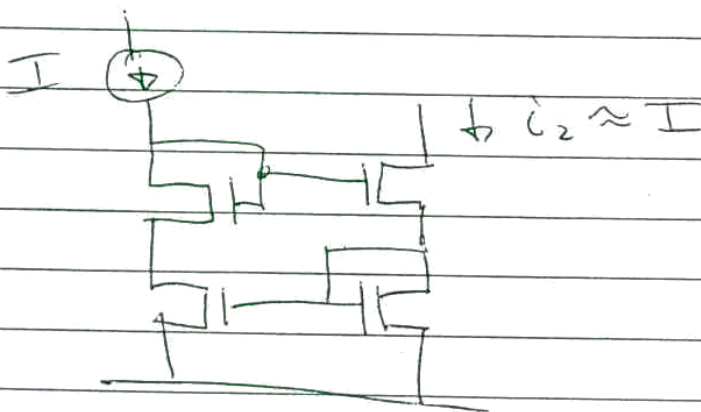

Note

9

"DIODE CONNECTED" FET

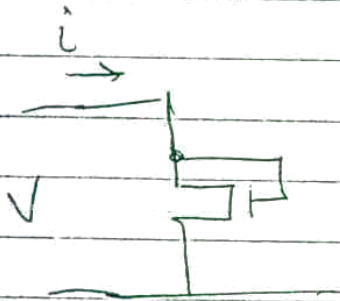


ABOVE V_T ; $V > V_T$
FET IS "ON" ($i > 0$)

BELOW V_T ; $V < V_T$
FET IS "OFF" ($i = 0$)

Differential Amplifier

(10)

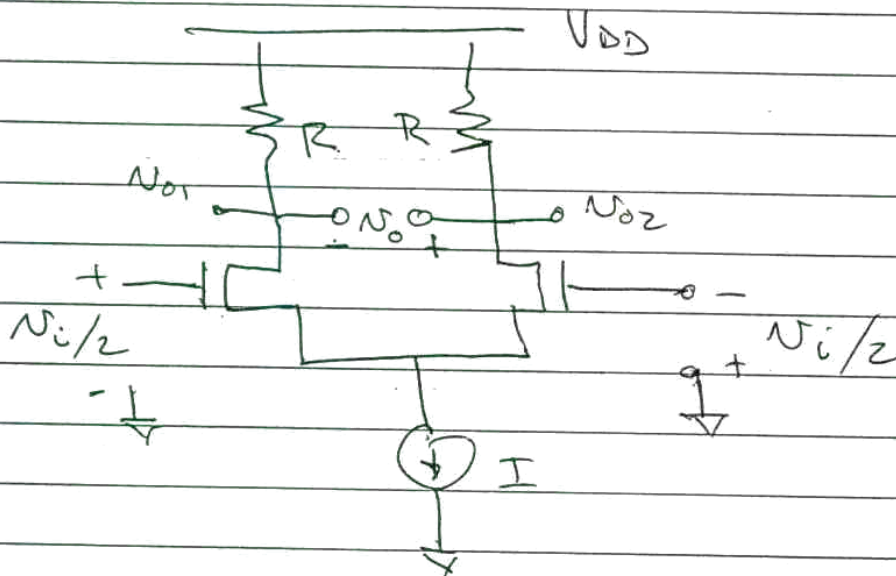

$$V_{o1} = -g_m (R \parallel r_o) \frac{V_i}{2}$$

$$V_{o2} = -g_m (R \parallel r_o) \left(-\frac{V_i}{2} \right)$$

$$r_o = \text{FET OUTPUT RESISTANCE} = \frac{1}{\lambda I_D} = \frac{2}{\lambda I}$$

$$V_o = V_{o2} - V_{o1} = g_m (R \parallel r_o) V_i$$

$$\text{DIFFER. GAIN} = \frac{V_o}{V_i} = g_m (R \parallel r_o)$$

$$\text{Recall } g_m \approx \frac{1}{L} k_p (V_{gs} - V_T) = \sqrt{2 \frac{W}{L} k_p I_D}$$

$$= \frac{2 I_D}{V_{gs} - V_T}$$

So

$$\text{DIFF GAIN} \approx \sqrt{\frac{W}{L}} I k_p (R \parallel r_o) = \frac{I (R \parallel r_o)}{V_{gs} - V_T}$$

$$\text{Since } r_o \approx \frac{2}{\lambda I}$$

(11)

$$\text{DIFF GAIN} = \frac{v_o}{v_i} = \frac{I(R \parallel r_o)}{V_{GS} - V_T} = \frac{I(R \parallel \frac{2}{\lambda I})}{V_{GS} - V_T}$$

$$\text{MAX GAIN IS } R \rightarrow \infty, R \parallel \frac{2}{\lambda I} \Rightarrow \frac{2}{\lambda I}$$

$$\text{MAX GAIN} = \frac{2}{\lambda (V_{GS} - V_T)}$$

Similarly

$$\text{DIFF GAIN} = \sqrt{\frac{\omega}{L} k_p I} (R \parallel r_o) = \sqrt{\frac{\omega}{L} k_p I} (R \parallel \frac{2}{\lambda I})$$

$$\text{MAX GAIN} \approx \sqrt{\frac{\omega}{L} k_p I} \left(\frac{2}{\lambda I} \right)$$

$$= \sqrt{4 \frac{\omega}{L} k_p \left(\frac{1}{I} \right) \left(\frac{1}{\lambda^2} \right)}$$


So Higher Gain

- INCREASE ω/L

- REDUCE I

Active Load

12

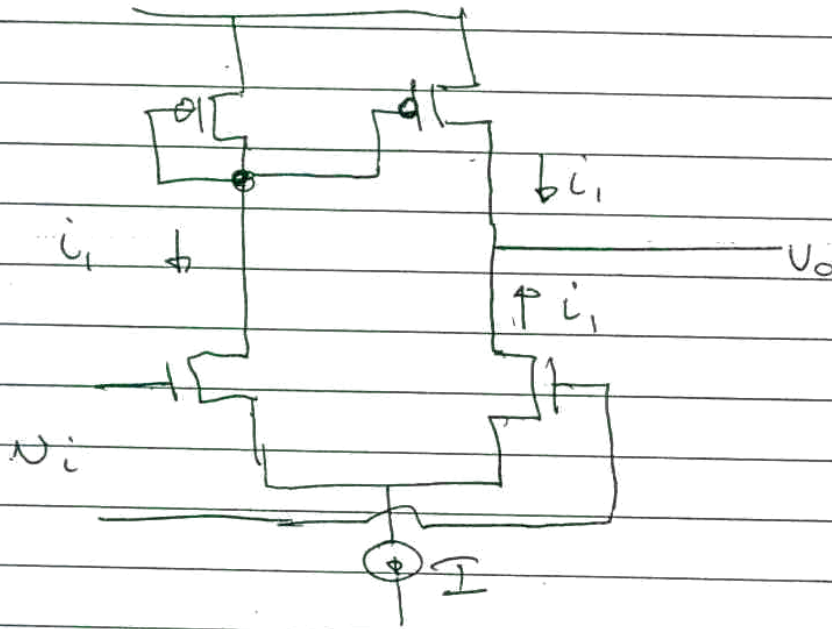

Current mirror drives i_1 down on right top
so get $2x$ current.

However, get $\frac{1}{2}$ voltage since out put here
isnt differential (it is single-ended)

So these two effects cancel


Finally $R = r_o$ since it is replaced
By the upper FET

$$\underline{\text{So}} \Rightarrow \text{GAIN} = \frac{V_o}{V_i} = g_m (r_o || r_o) = g_m \frac{r_o}{2}$$

$$= \frac{1}{\lambda (V_{gs} - V_T)} = \frac{1}{\lambda I} \sqrt{\frac{W}{L} k_P I}$$

$$= \sqrt{\frac{W}{L} k_P} \left(\frac{1}{\lambda^2 I} \right)$$

Implementation

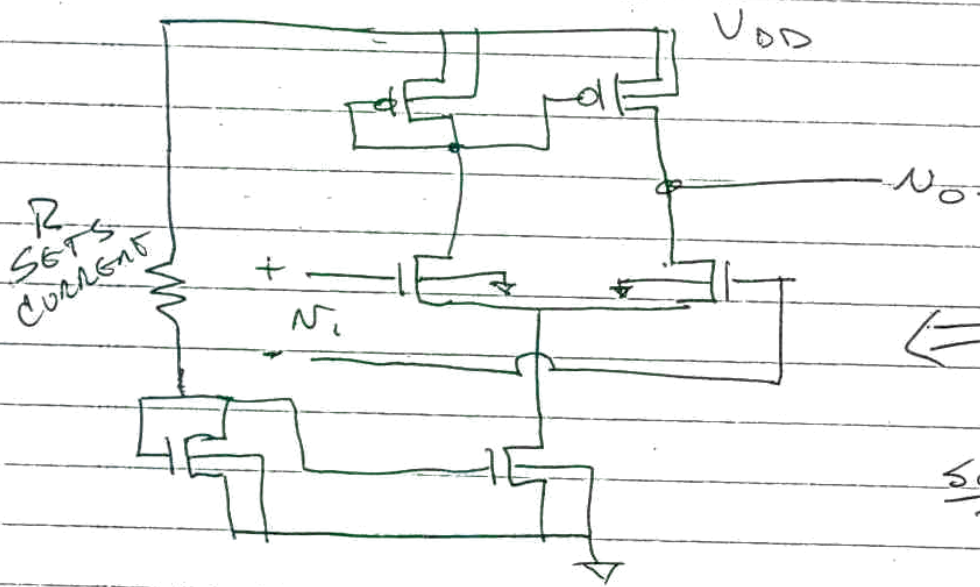

← NFETS MUST HAVE BULK GROUNDING IN OUR PROCESS
SO BULK EFFECT ON V_T

BETTER




ALL DEVICES BULK CONNECTED TO SOURCE.

Finally

14

ADD SOURCE FOLLOWER w/ a choe load

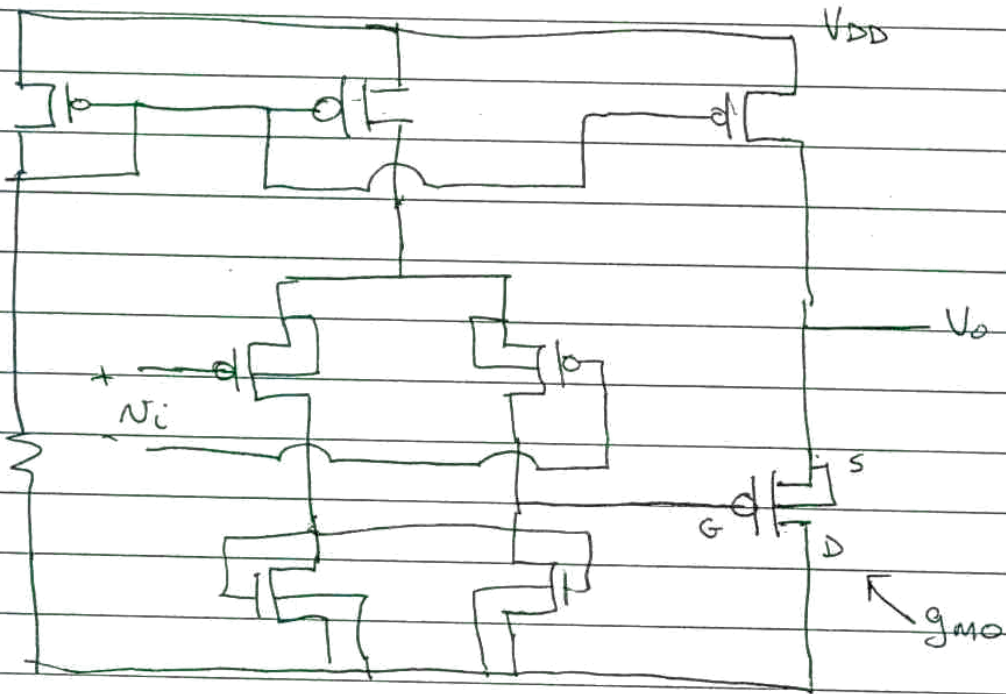

SOURCE FOLLOWER

$$GAIN \approx 1$$

$$R_{OUT} \approx \frac{1}{g_{m0}}$$

⇒ LOWER OUTPUT IMPEDANCE


⇒ LARGER BANDWIDTH.

(DRIVING CAPACITANCE.)

Simple Bias Scheme

BIAS


Amplifier

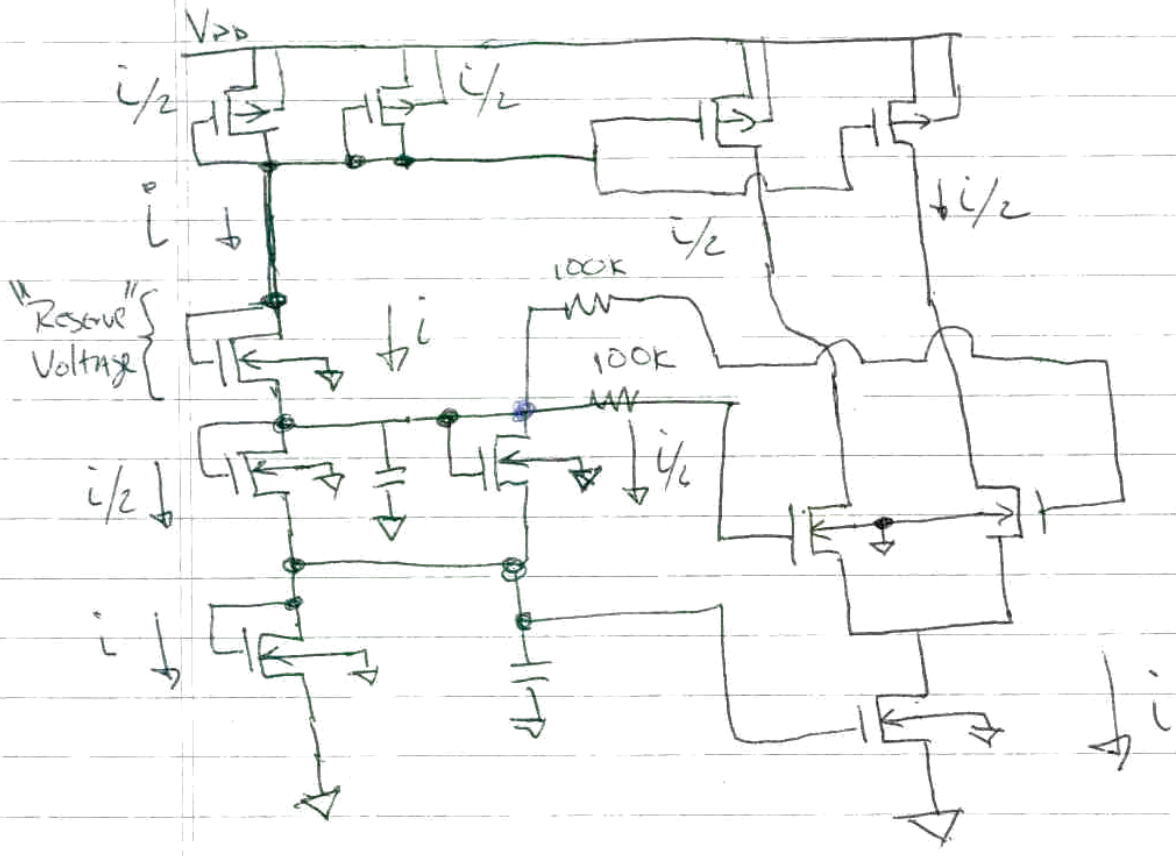

BJT

(15)

NPN

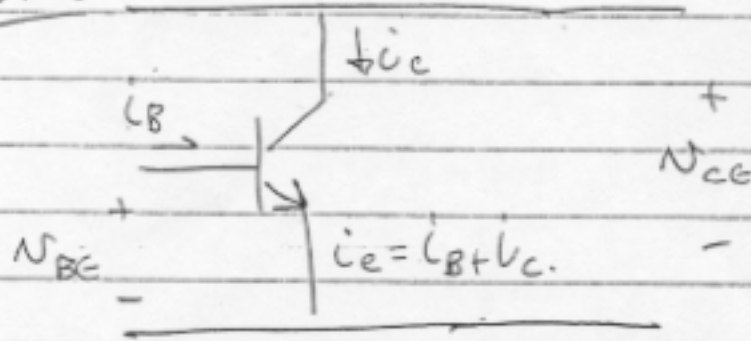


$$i_c = I_s e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right); V_T = \frac{kT}{q} = 0.025V$$

Also $i_c = \beta i_B = \alpha i_e$ $\alpha = \frac{\beta}{\beta + 1}$

Typical $\beta = 100$ $I_s = 10^{-15}$ Amp.

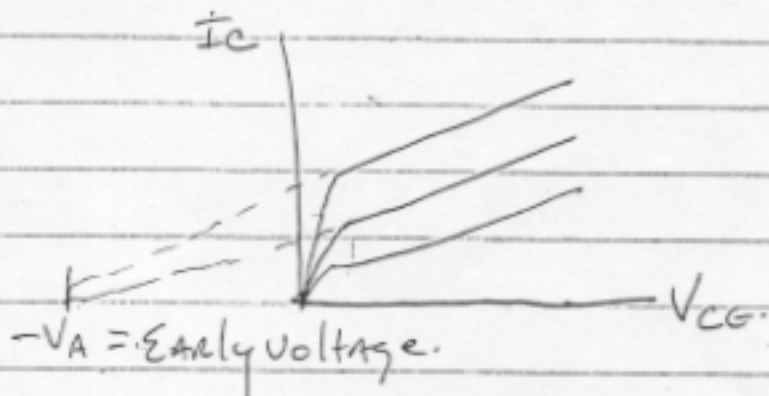In Normal Operation $V_{BE} \approx 0.7V_{DC}$




$$i_c = I_s e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$r_o \approx \frac{V_A}{i_c}$$

DC Analysis

16

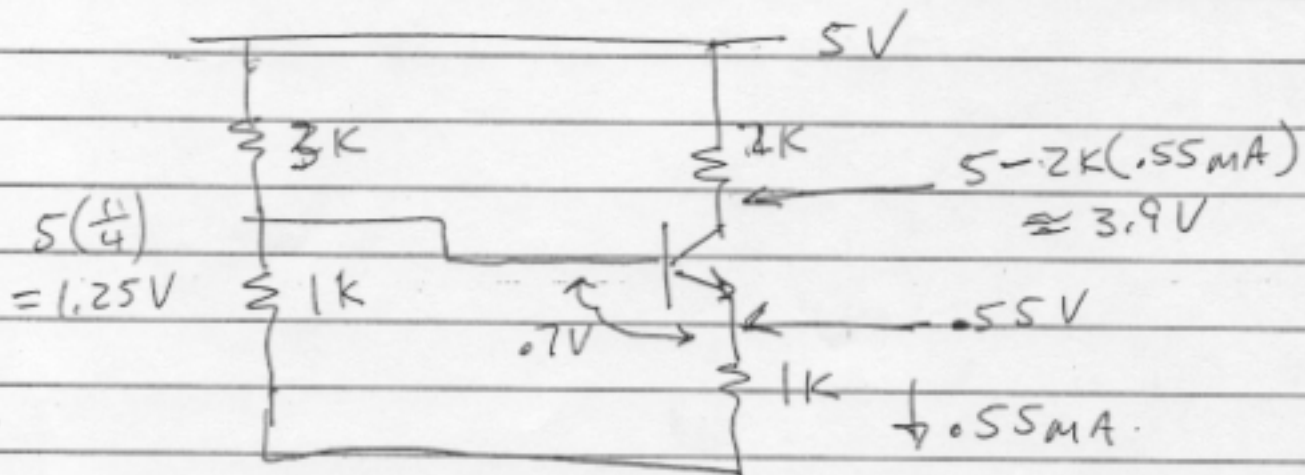

① Find Base Voltage


② Emitter = Base - 0.7V.

③ Find Emitter current
= Emitter Voltage / Resistor Value.


④ Find Collector Voltage
= 5V - (Collector Resistance)(Emitter Current)

DIODE CONNECTED BJT

Usually

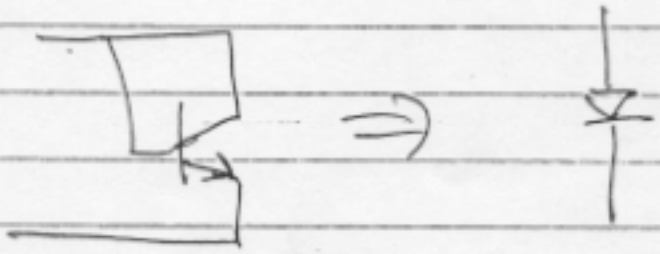

Small Signal Model

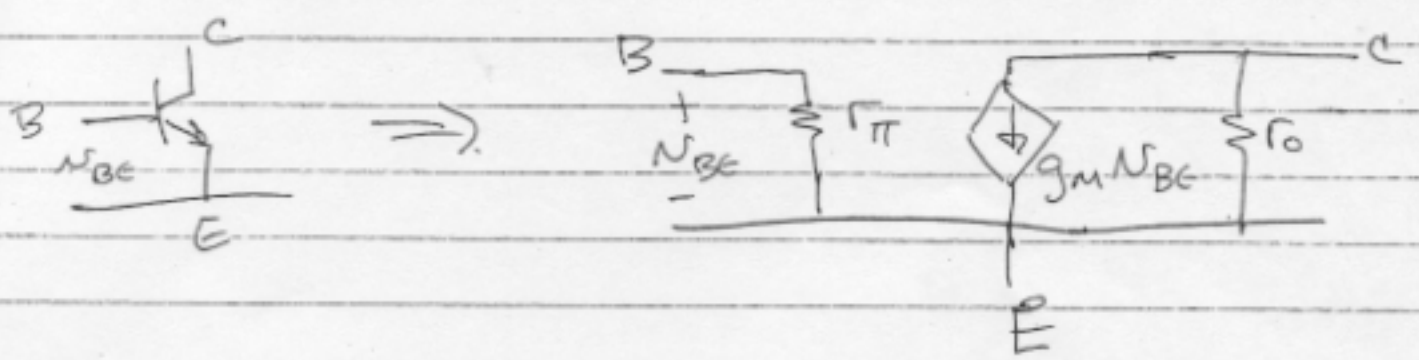

$$g_m = \frac{dI_c}{dV_{BE}} \approx \frac{d}{dV_{BE}} I_{se}^{N_{BE}/V_T} = \frac{1}{V_T} I_{se}^{N_{BE}/V_T}$$

$$g_m \approx \frac{I_c}{V_T} \leftarrow \text{DC collector current}$$

$$\frac{1}{r_{\pi}} = \frac{d\beta}{dV_{BE}} = \frac{1}{\beta} \frac{dI_c}{dV_{BE}} = g_m / \beta$$

So $r_{\pi} = \beta / g_m$.

And $r_o = V_A / I_c$ AS BEFORE

BJT High FREQ Model


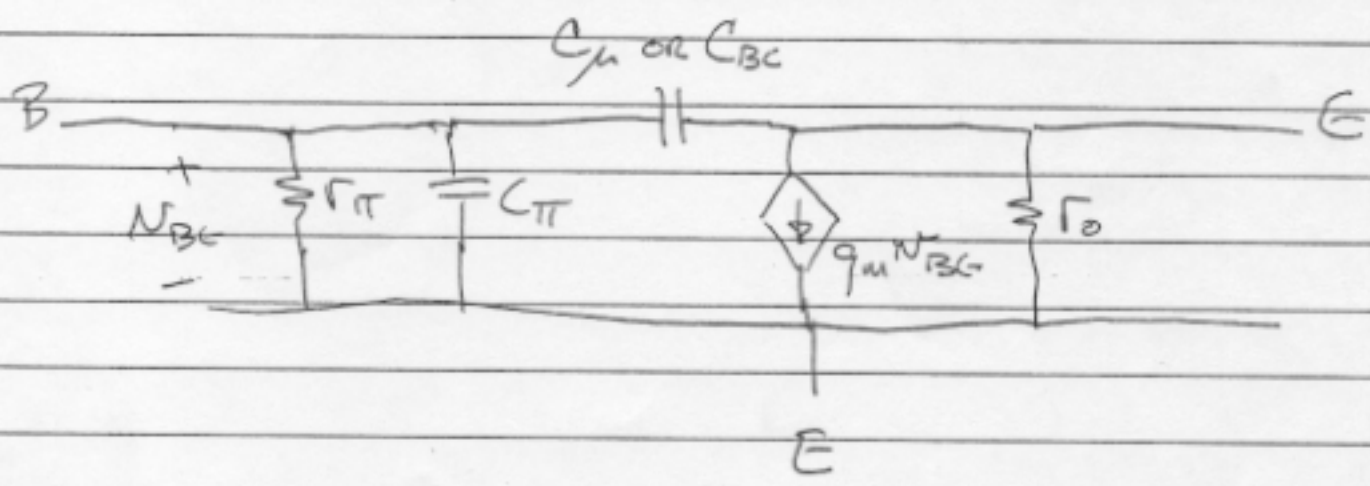


FIGURE OF MERIT

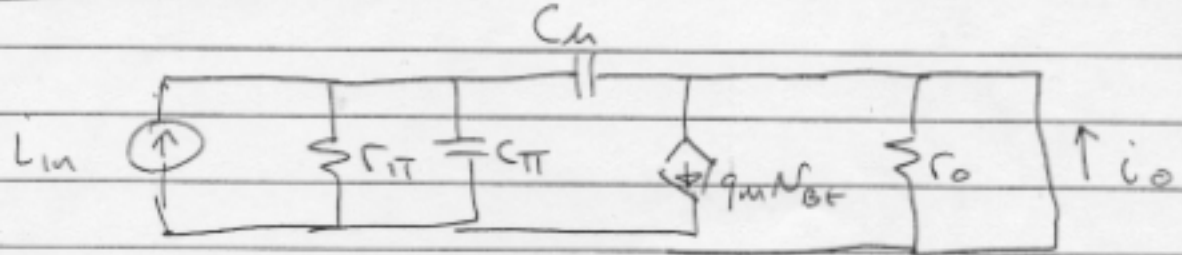

$$i_o = g_m N_{BC} = g_m i_{in} \left(r_{\pi} \parallel \left(\frac{1}{s(C_{\pi} + C_{\mu})} \right) \right)$$

Solve $\frac{i_o}{i_{in}} = \frac{g_m r_{\pi}}{1 + s r_{\pi} (C_{\pi} + C_{\mu})}$ ← β / g_m


$$= \frac{\beta}{1 + s r_{\pi} (C_{\pi} + C_{\mu})}$$

Unity CURRENT GAIN AT (Assuming $\beta \gg 1$)

CUTOFF FREQUENCY $\omega_T = 2\pi f_T = \frac{\beta}{r_{\pi} (C_{\pi} + C_{\mu})} = \frac{g_m}{C_{\pi} + C_{\mu}}$

$$= \frac{I_c / V_T}{C_{\pi} + C_{\mu}}$$

BJT DIFFERENTIAL AMP.

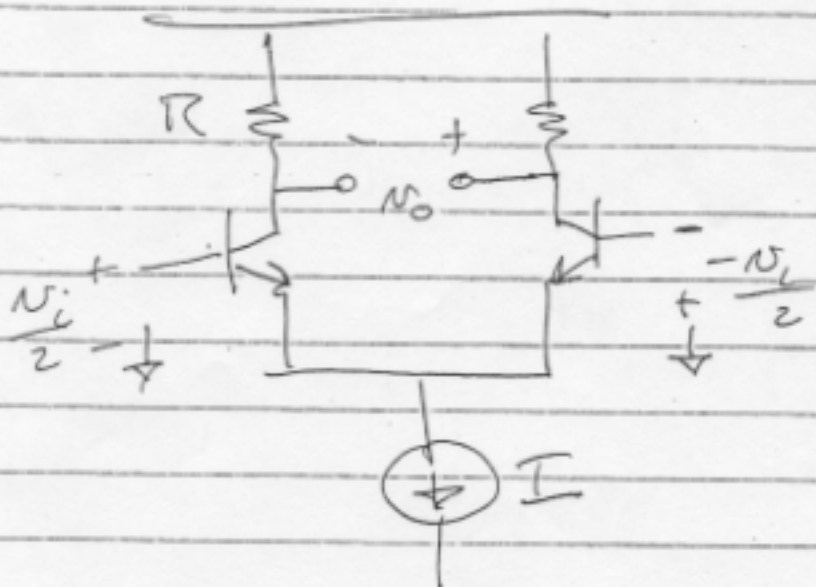


SAME ANALYSIS AS FET.

$$\text{DIFF GAIN} = \frac{N_o}{N_i} = g_m (R || r_o)$$

NO BJT ACTIVE LOAD IN OUR PROCESS, SINCE WE DONT HAVE PNP DEVICES!


HOWEVER, YOU CAN USE A FET ACTIVE LOAD

BJT Diff Amp w/ Fet Active Load

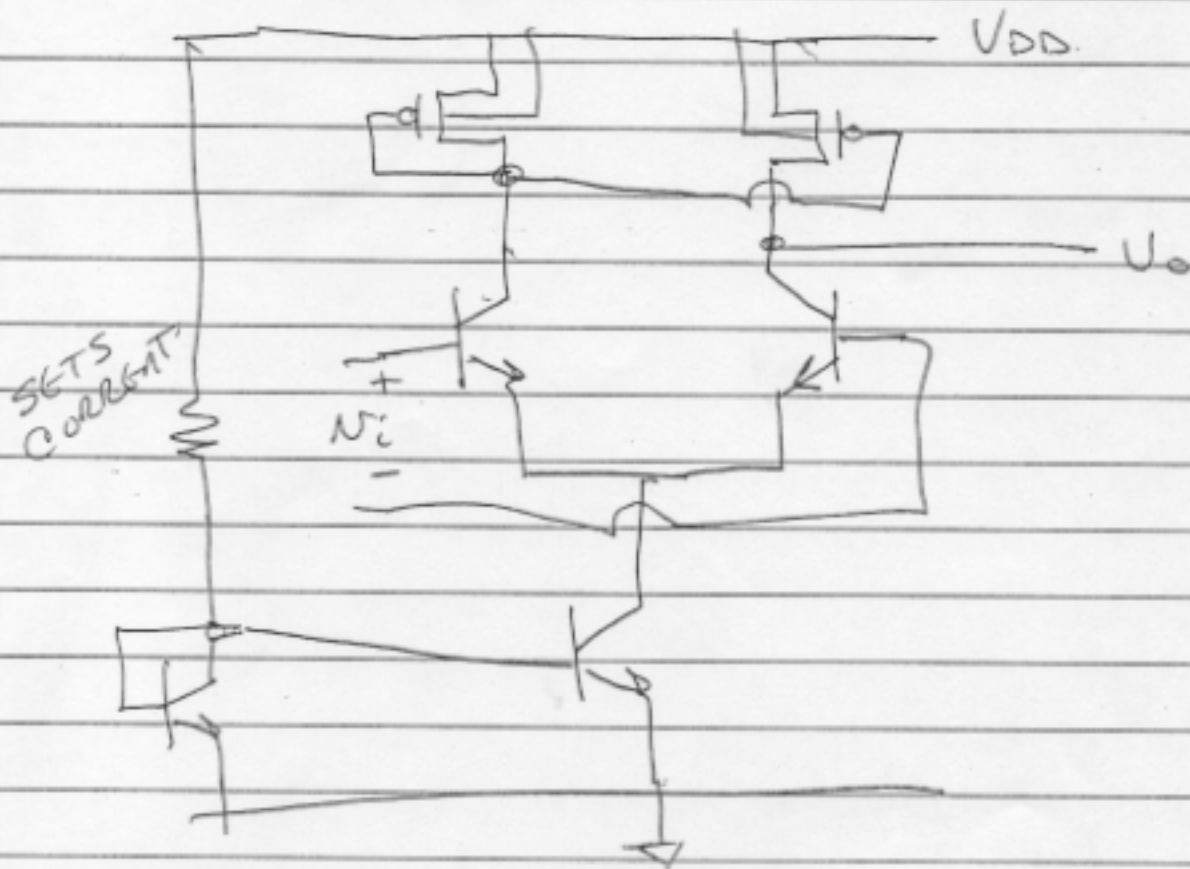

MILLER EFFECT


(21)

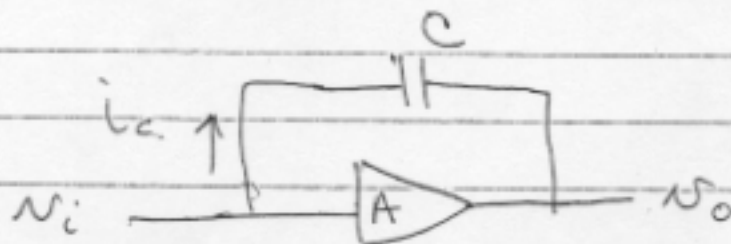

$$N_o = A N_i$$

$$i_c = \frac{N_i - N_o}{X_c} = \frac{N_i(1-A)}{X_c} = \frac{N_o\left(\frac{1}{A} - 1\right)}{X_c}$$

SAME AS.

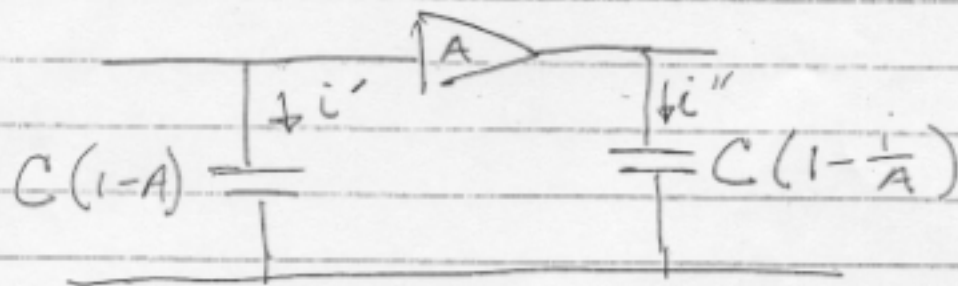

Check

$$i' = \frac{N_i}{\frac{1}{j\omega C(1-A)}} = \frac{N_i}{\frac{1}{j\omega C(1-A)}} = \frac{N_i(1-A)}{X_c} \checkmark$$

$$i'' = \frac{N_o}{\frac{1}{j\omega C\left(1-\frac{1}{A}\right)}} = \frac{N_o\left(1-\frac{1}{A}\right)}{X_c} \checkmark$$

SO SAME CURRENTS DRAINED FROM BOTH PORTS.


NOTE A IS USUALLY NEGATIVE

High Frequency Modeling

22


FET

Common Source.

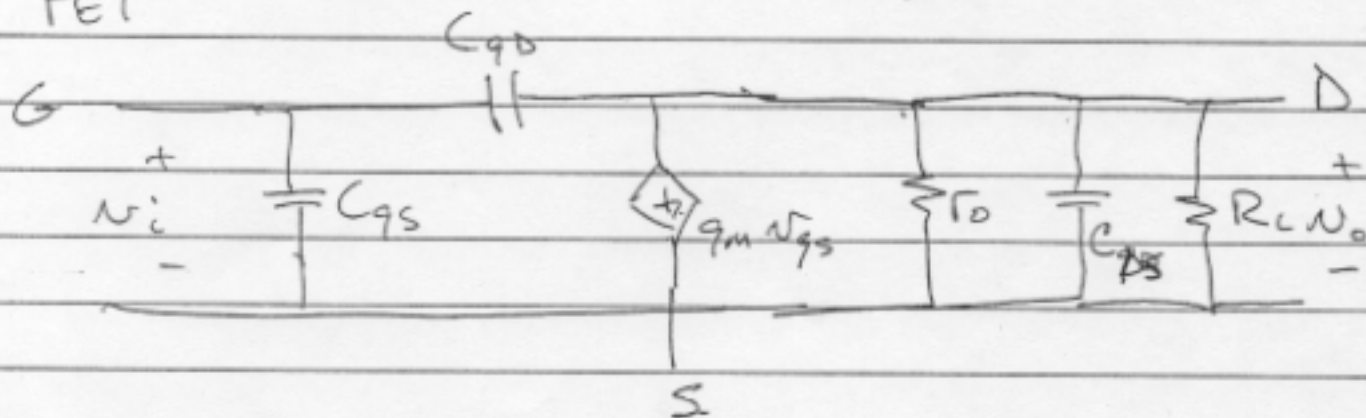

$$\text{GAIN (IGNORING } C_{gd}) = \frac{v_o}{v_i} = -g_m (r_o \parallel R_L) = A$$

Then use Miller Effect.

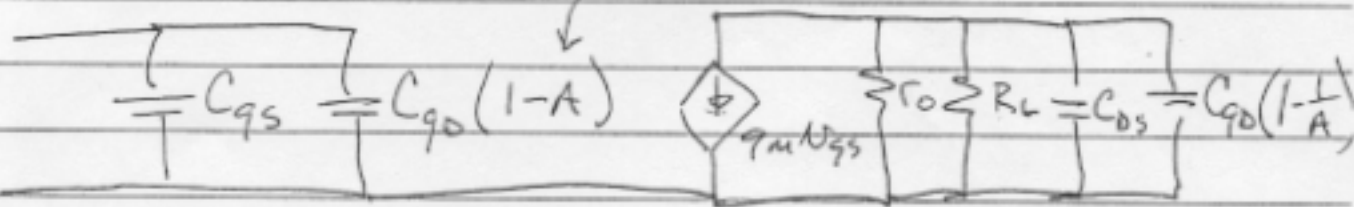


Simplifies Analysis

Note FOR LARGE GAIN A ,
this LEADS TO LARGE CAPACITANCE

\Rightarrow MULTIPLIES C_{gd} !!

BJT High Freq.

23

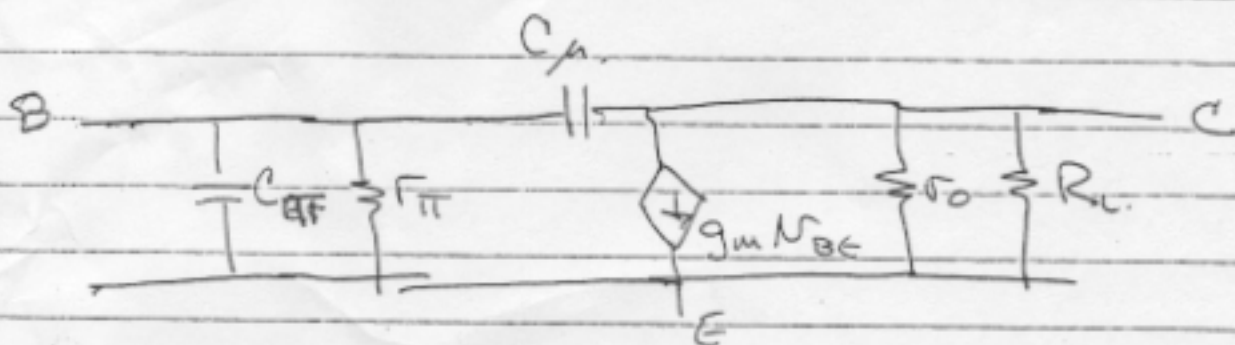

Gain (without Caps) $\frac{V_o}{V_i} = -g_m (r_o || R_L) = A$

THEN USE MILLER EFFECT

