

Name: _____

Student Number: _____

Do NOT begin until told to do so

Make sure that you have all pages before starting

Open notes

DO ALL WORK ON THE SPACE GIVEN

Do NOT use the back of the pages, do NOT turn in extra sheets of work/paper

Multiple-choice answers should be within 5% of correct value

Show all work, even for multiple choice

ACADEMIC INTEGRITY:

Students have the responsibility to know and observe the requirements of The UNCC Code of Student Academic Integrity (1999-2001 Catalog page 375). This code forbids cheating, fabrication or falsification of information, multiple submission of academic work, plagiarism, abuse of academic materials, and complicity in academic dishonesty.

Unless otherwise noted:

 $F\{\}$ denotes Fourier transform $F^{-1}\{\}$ denotes inverse Fourier transform ω denotes frequency in rad/s

* denotes linear convolution

 $x^*(t)$ denotes the conjugate of $x(t)$

Useful constants, etc:

$e \approx 2.72$

$1/e \approx 0.37$

$\sqrt{3} \approx 1.73$

$\sqrt{7} \approx 2.64$

$\ln(2) \approx 0.69$

$\log_{10}(2) \approx 0.30$

$\log_{10}(10) \approx 1.0$

$\log_{10}(e) \approx 0.43$

$\pi \approx 3.14$

$\sqrt{2} \approx 1.41$

$\sqrt{5} \approx 2.22$

$\sqrt{10} \approx 3.16$

$\ln(4) \approx 1.38$ &

$\log_{10}(3) \approx 0.48$ &

$\log_{10}(0.1) \approx -1$

$\cos(\pi/4) \approx 0.71$

$\cos(A) \cos(B) = 0.5 \cos(A - B) + 0.5 \cos(A + B)$

$e^{j\theta} = \cos(\theta) + j \sin(\theta)$

5 Points each

5 Points Each

1. Maximum power transfer occurs when the load impedance is the conjugate of the source impedance.
a) True b) False

2. The angle of the reflection coefficient, Γ , of a short circuit is
a) 0° b) 90° c) 120° d) none above

3. If a 50 ohm source sends a +5 volt pulse down a 50 ohm transmission line terminated in 25 ohms, the polarity of the reflected pulse will be positive.
a) True b) False

4. An impedance of $1 + j 1$ ohms is equivalent to an admittance of
a) $0.5 + j0.5$ b) $1 - j 1$ c) $0.2 + j 0.2$ d) none above

5 Points each

5. The percentage of incident power delivered to a load with VSWR=3 is

- a) 25% b) 33% c) 89% d) none above

6. The return loss of a 150 ohm resistor in a $Z_0=50$ ohm system is

- a) 0 dB b) 6 dB c) 9.5 dB d) none above

7. An amplifier with source and load impedances of Z_0 and with $s_{21} = 2$ has a transducer gain of

- a) 3 dB b) -3 dB c) 6 dB d) none above

8. The impedance of a 50 ohm, $3/4 \lambda$ length, transmission line terminated by a short circuit is

- a) $-j 25 \Omega$ b) $j 50 \Omega$ c) $\infty \Omega$ d) none above

5 Points each

9. The maximum transducer gain possible for a 2-port in dB is $10\log_{10}(|s_{21}|^2)$

- a) True b) False

10. A transmission line is measured to have a capacitance of 1000 pF/m and inductance of 100 nH/m, the impedance of the line is.

- a) 10 Ω b) 50 Ω c) 100 Ω d) none above

11. A transmission line is measured to have a capacitance of 1000 pF/m and inductance of 100 nH/m, the velocity of the line is.

- a) 10^8 m/s b) 2×10^8 m/s c) 3×10^8 m/s d) none above

12. The cascade noise figure of a 1 dB attenuator followed by an amplifier with 3 dB noise figure and 40 dB gain is:

- a) 1dB b) 3 dB c) 43 dB d) none above

5 Points each

13. The impedance of a 0.5 micron wide microstrip line on a SiO_2 dielectric of thickness 1 micron and dielectric constant 4 is

- a) 36Ω b) 74Ω c) 50Ω d) none above

14. A 7 dBm signal in 50 ohms is

- a) 1 Vrms b) 3.3 Vrms c) 10 Vrms d) none above

15. A -3 dBv signal in 50 ohms is

- a) 10 dBm b) -3 dBm c) -20 dBm d) none above

16. The effective output noise in a 1 MHz bandwidth at the input of an amplifier with 20 dB gain, 4 dB noise figure is

- a) -150 dBm b) -100 dBm c) -90 dBm d) none above

5 Points each

For the following questions, assume $Z_0=50$ ohms, and use the Smith chart and select the closest answer.

17. For $Z= 75 + j75$, $|\Gamma| =$

- a) .25 b) .35 c) .45 d) .54

18. For $Z= 75 + j75$, $\angle \Gamma =$

- a) -116° b) -58° c) 40° d) 116°

19. For $Z= 75 + j75$, $|S_{11}| =$

- a) .14 b) .38 c) .45 d) .54

20. For $Z= 75 + j75$, $Y_n =$

- a) $0.33 - j0.33$ b) $0.5 - j2$ c) $0.5 + j2$ d) $0.5 - j 0.5$

21. For $Z= 75 + j75$, return loss =

- a) 5.2 dB b) 7.1 dB c) 9 dB d) 14 dB

25 Points

22. Three devices are cascaded in a system. Fill in the cascade analysis table as shown in class.

NOTE: the analysis for IP3 and P1dB are OUTPUT IP3 and OUTPUT P1dB of the stages and cascades!!!


STAGE	Filter		Amp1		Amp2	
gain,dB	-3.0		7.0		20.0	G
nf,dB	3.0		7.0		20.0	NF
OIP3, dBm	50.0		15.0		30.0	OIP3
Output P1dB, dBm	50.0		0.0		20.0	P1dB
TOTAL						
gain,dB	-3.0					G
nf,dB	3.0					NF
OIP3,dBm	50.0					IP3
P1dB out, dBm	50.0					1dB

10 Points Each

On the Smith chart below, assume $Z_0=50$ ohm.

23. Show the location of $Z=100 + j 10$ ohms as an "X" on the Smith chart below.


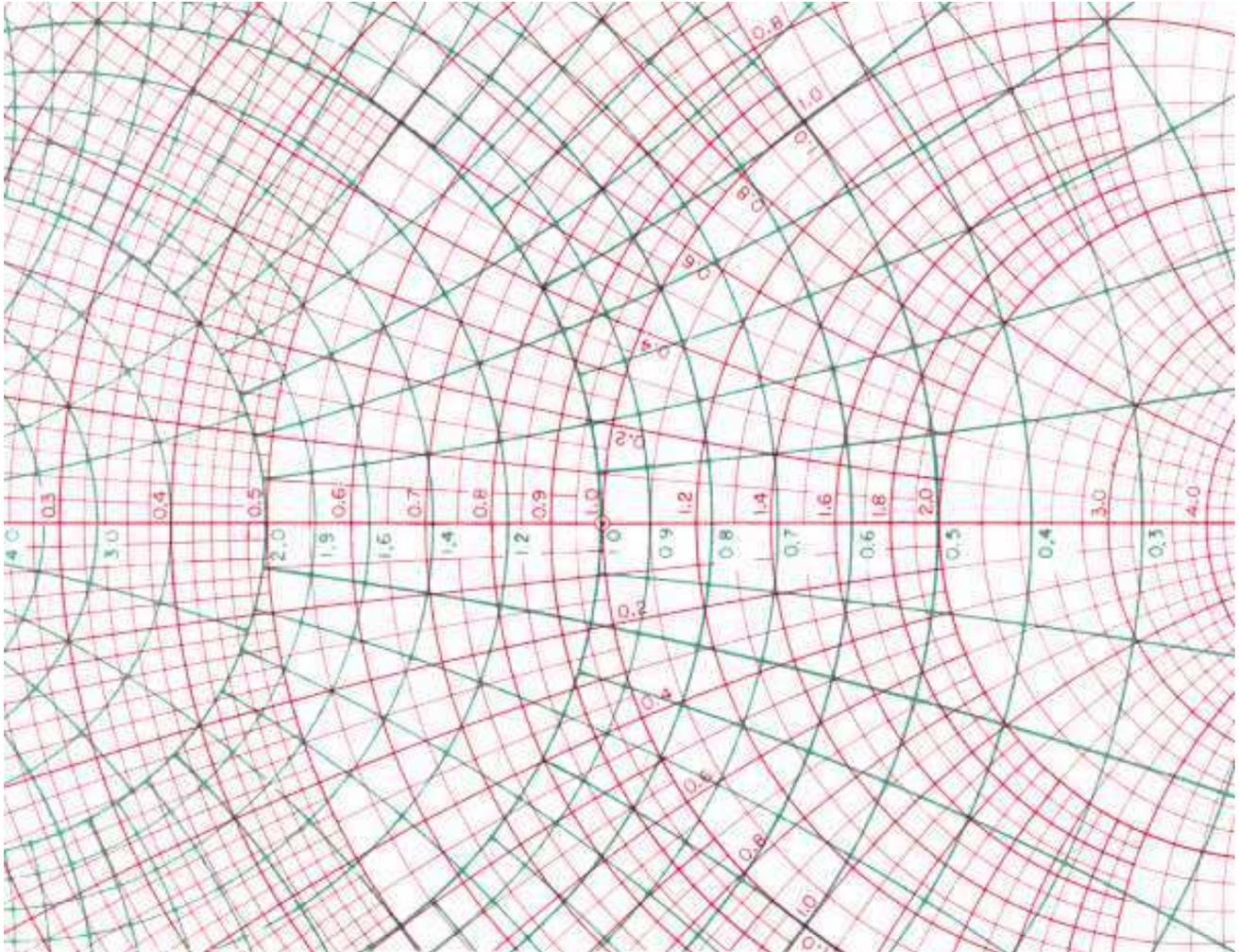
24. Show the location of $Y = 0.3 + j 0.1$ ohms as an "O" on the Smith chart below.



On the Smith chart below, assume $Z_0=50$ ohm.

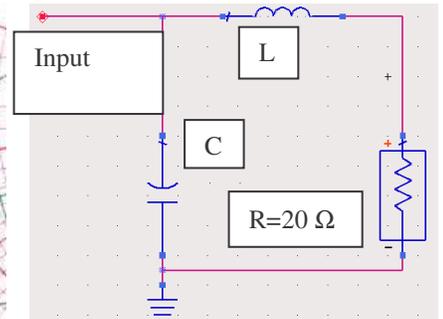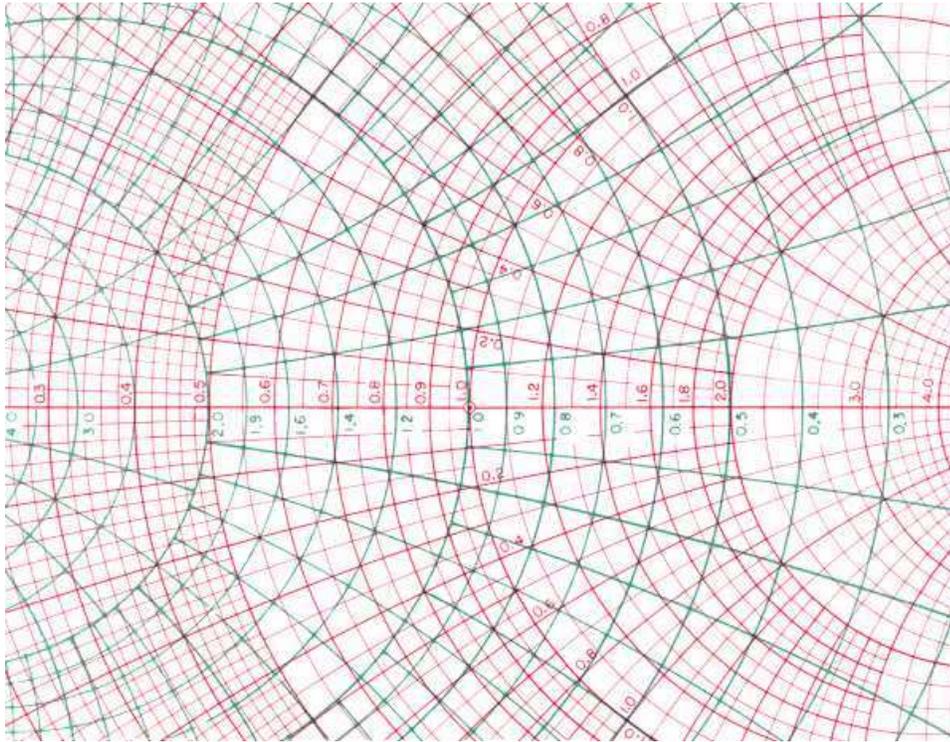25. (20 Points)

Draw the paths (for L and C) on the Smith chart corresponding to the matching network of the circuit shown below. The circuit matches the 20 ohm termination R into **25** ohms.



5 Points each

26. In the above circuit, the Normalized impedance of the inductor in the matching circuit $Z_n =$


- a) $j1$ b) $j0.2$ c) $j0.5$ d) $0.5 + j0.5$

27. In the above circuit, the Normalized Admittance of the capacitor in the matching circuit $Y_n =$

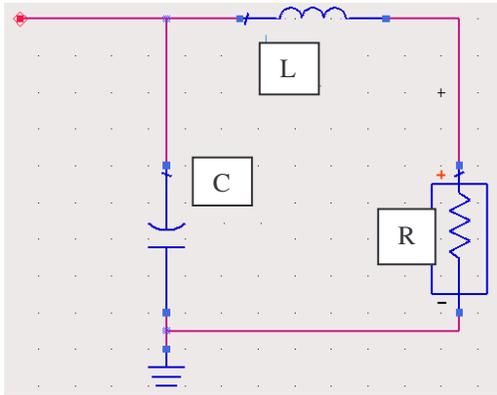- a) $j1$ b) $-j1$ c) $1 - j1$ d) $0.5 + j0.5$

5 Points Each

In the circuit below, the normalized impedances of the inductor L is $Z_n = j 0.5$, and the normalized impedance of the capacitor C is $Z_n = -j 2$, where $Z_0=50$ ohms. The frequency is 1000 MHz.



28. In the above circuit, the value the capacitor (within 5%) in the matching circuit is

- a) 160 pF b) 1.6 pF c) 3.2 pF d) none above

29. In the above circuit, the value the inductor (within 5%) in the matching circuit is

- a) 0.39 nH b) 3.8 nH c) 8 nH d) none above