

Name: _____

Student Number: _____

Do NOT begin until told to do so

Make sure that you have all pages before starting

Open notes

DO ALL WORK ON THE SPACE GIVENDo **NOT** use the back of the pages, do **NOT** turn in extra sheets of work/paper

Multiple-choice answers should be within 5% of correct value

Show all work, even for multiple choice**ACADEMIC INTEGRITY:**

Students have the responsibility to know and observe the requirements of The UNCC Code of Student Academic Integrity. This code forbids cheating, fabrication or falsification of information, multiple submission of academic work, plagiarism, abuse of academic materials, and complicity in academic dishonesty.

Unless otherwise noted:

 $F\{\}$ denotes Fourier transform $F^{-1}\{\}$ denotes inverse Fourier transform ω denotes frequency in rad/s

* denotes linear convolution

 $x^*(t)$ denotes the conjugate of $x(t)$

Useful constants, etc:

$e \approx 2.72$

$1/e \approx 0.37$

$\sqrt{3} \approx 1.73$

$\sqrt{7} \approx 2.64$

$\ln(2) \approx 0.69$

$\log_{10}(2) \approx 0.30$

$\log_{10}(10) \approx 1.0$

$\log_{10}(e) \approx 0.43$

$\pi \approx 3.14$

$\sqrt{2} \approx 1.41$

$\sqrt{5} \approx 2.22$

$\sqrt{10} \approx 3.16$

$\ln(4) \approx 1.38$ &

$\log_{10}(3) \approx 0.48$ &

$\log_{10}(0.1) \approx -1$

$\cos(\pi/4) \approx 0.71$

$\cos(A) \cos(B) = 0.5 \cos(A - B) + 0.5 \cos(A + B)$

$e^{j\theta} = \cos(\theta) + j \sin(\theta)$

5 Points Each

1. The center of the Smith chart is always 50 ohms impedance.

- a) True b) False

2. An impedance of $1 + j3$ ohms is equivalent to an admittance of

- a) $0.3 + j0.1$ b) $0.1 - j0.3$ c) $0.3 - j0.1$ d) none above

3. The percentage of incident power delivered to a load with 7 dB return loss is

- a) 20% b) 63% c) 80% d) none above

4. The return loss of a 200 ohm resistor in a $Z_0=50$ ohm system is

- a) 2.1 dB b) 4.4 dB c) 6 dB d) none above

5 Points each

5. The angle of the reflection coefficient, Γ , of a capacitor with 50 ohm reactance is

- a) -90° b) 90° c) 120° d) none above

6. If a +5 volt pulse travels down a 50 ohm transmission line terminated in 25 ohms, the polarity of the reflected pulse from the load will be positive.

- a) True b) False

7. An amplifier with source and load impedances of Z_0 and with $s_{21} = 5$ has a transducer gain of

- a) 7 dB b) 14 dB c) 21 dB d) none above

8. The impedance of a 100 ohm, $1/4 \lambda$ length, transmission line terminated by a short circuit is

- a) $-j 100 \Omega$ b) $j 50 \Omega$ c) $j100 \Omega$ d) none above

5 Points each

9. The maximum transducer gain possible for a 2-port in dB is $10\log_{10}(|s_{21}|^2)$

- a) True b) False

10. A transmission line is measured to have a capacitance of 300 pF/m and inductance of 100 nH/m, the impedance of the line is.

- a) 18 Ω b) 30 Ω c) 150 Ω d) none above

11. A transmission line is measured to have a capacitance of 300 pF/m and inductance of 100 nH/m, the velocity of the line is.

- a) 10^8 m/s b) 1.8×10^8 m/s c) 3×10^8 m/s d) none above

12. The cascade noise figure of a 2 dB attenuator followed by an amplifier with 4 dB noise figure and 25 dB gain is:

- a) 6dB b) 29 dB c) 31 dB d) none above

5 Points each

13. A 1 Watt signal in 50 ohms is

- a) 1 Vrms b) 3.3 Vrms c) 7 Vrms d) none above

14. A -6 dBv signal in 50 ohms is

- a) 7 dBm b) -6 dBm c) -23 dBm d) none above

15. The effective output noise in a 10 MHz bandwidth of an amplifier with 10 dB gain, 4 dB noise figure is

- a) -150 dBm b) -100 dBm c) -90 dBm d) none above

16. The effective dielectric constant of a 0.5 micron wide microstrip line on a SiO₂ dielectric of thickness 1 micron and dielectric constant 4 is

- a) 2.8 b) 3.1 c) 4 d) none above

5 Points each

For the following questions, assume $Z_0=50$ ohms, and use the Smith chart and select the closest answer.

17. For $Z= 25 + j50$, $|\Gamma| =$

- a) .25 b) .35 c) .45 d) .62

18. For $Z= 25 + j50$, $\angle \Gamma =$

- a) 83° b) -58° c) 40° d) 116°

19. For $Z= 25 + j50$, $|S_{11}| =$

- a) .14 b) .38 c) .54 d) .62

20. For $Z= 25 + j50$, $Y_n =$

- a) $0.4 - j0.8$ b) $0.5 - j2$ c) $0.8 + j.4$ d) $0.5 - j 0.5$

21. For $Z= 25 + j50$, return loss =

- a) 4.1 dB b) 7.1 dB c) 9 dB d) 14 dB

25 Points

22. Three devices are cascaded in a system. Fill in the cascade analysis table as shown in class.

NOTE: the analysis for IP3 and P1dB are OUTPUT IP3 and OUTPUT P1dB of the stages and cascades!!!


| STAGE | Filter | | Amp1 | | Amp2 | |
|------------------|--------|--|------|--|------|------|
| gain,dB | -6.0 | | 10.0 | | 20.0 | G |
| nf,dB | 6.0 | | 4.0 | | 20.0 | NF |
| OIP3, dBm | 50.0 | | 13.0 | | 30.0 | OIP3 |
| Output P1dB, dBm | 50.0 | | 0.0 | | 20.0 | P1dB |
| | | | | | | |
| | | | | | | |
| TOTAL | | | | | | |
| gain,dB | -6.0 | | | | | G |
| nf,dB | 6.0 | | | | | NF |
| OIP3,dBm | 50.0 | | | | | IP3 |
| P1dB out, dBm | 50.0 | | | | | 1dB |

10 Points Each

On the Smith chart below, assume $Z_0=50$ ohm.

23. Show the location of $Z=25 - j 20$ ohms as an "X" on the Smith chart below.


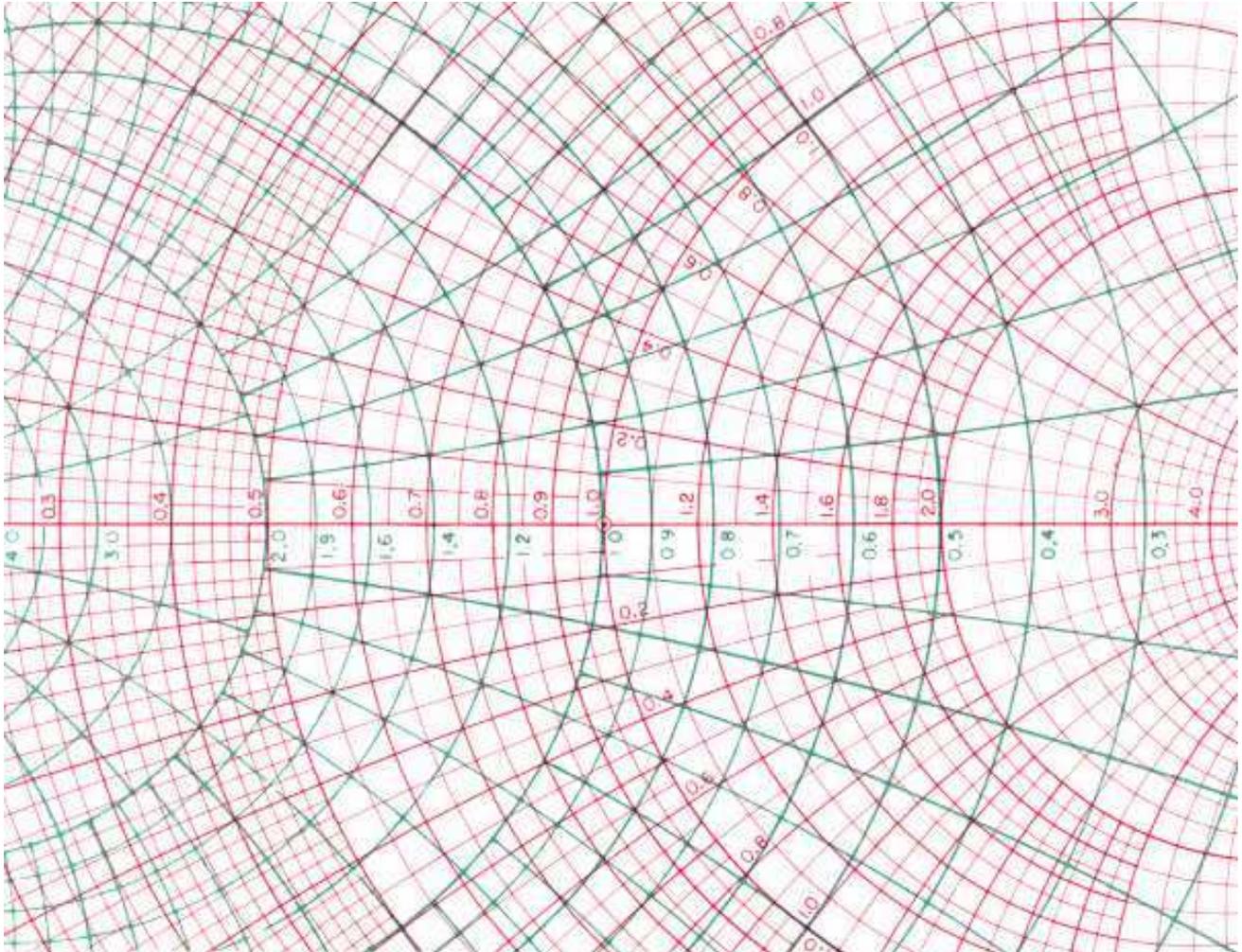
24. Show the location of $Y_n = 2 - j 0.5$ as an "O" on the Smith chart below.



On the Smith chart below, assume $Z_0=50$ ohm.

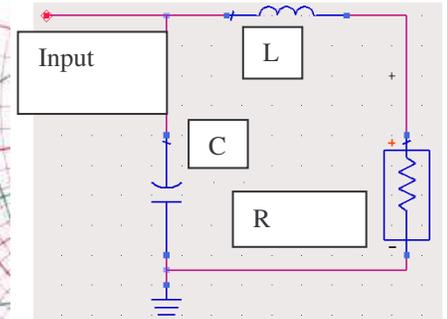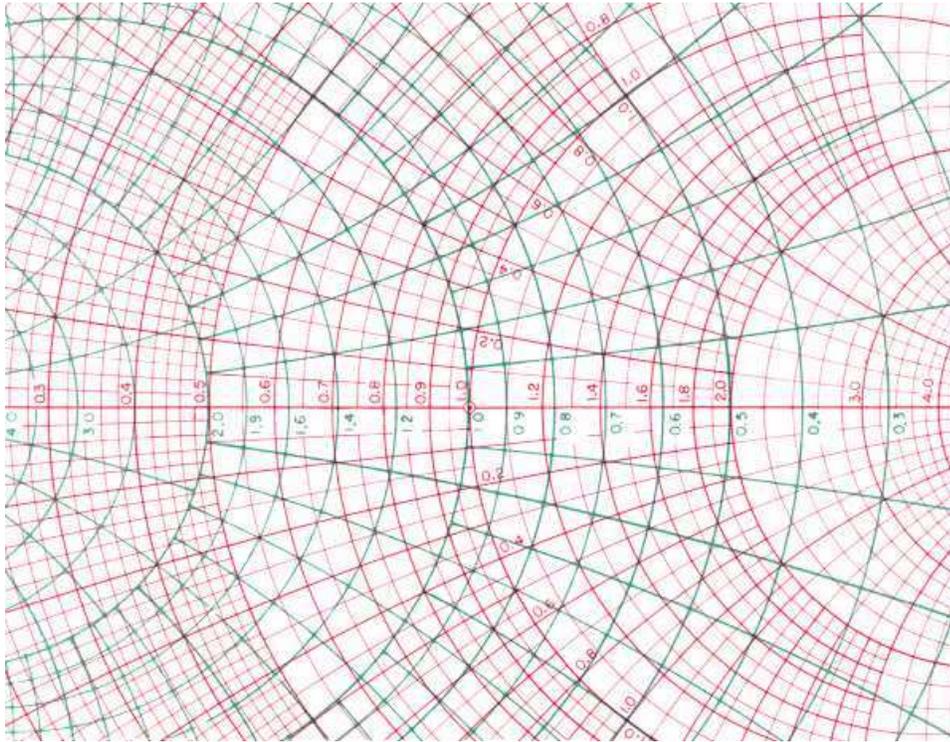25. (20 Points)

Draw the paths (for L and C) on the Smith chart corresponding to the matching network of the circuit shown below. The circuit matches the 20 ohm termination R into **50** ohms.



5 Points each


26. In the above circuit, the Normalized impedance of the inductor in the matching circuit $Z_n =$

- a) $j1$ b) $j0.21$ c) $j0.46$ d) $0.5 + j0.5$

27. In the above circuit, the Normalized Admittance of the capacitor in the matching circuit $Y_n =$

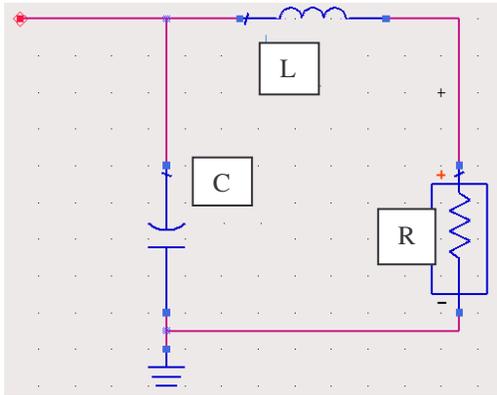- a) $j.9$ b) $-j.9$ c) $j1.1$ d) $0.5 + j0.5$

In the circuit below, the normalized impedances of the inductor L is $Z_n = j 1.5$, and the normalized admittance of the capacitor C is $Y_n = j 0.5$, where $Z_0=50$ ohms. The frequency is 1000 MHz.



5 Points Each


28. In the above circuit, the value the capacitor (within 5%) in the matching circuit is

- a) 160 pF b) 1.6 pF c) 3.2 pF d) none above

29. In the above circuit, the value the inductor (within 5%) in the matching circuit is

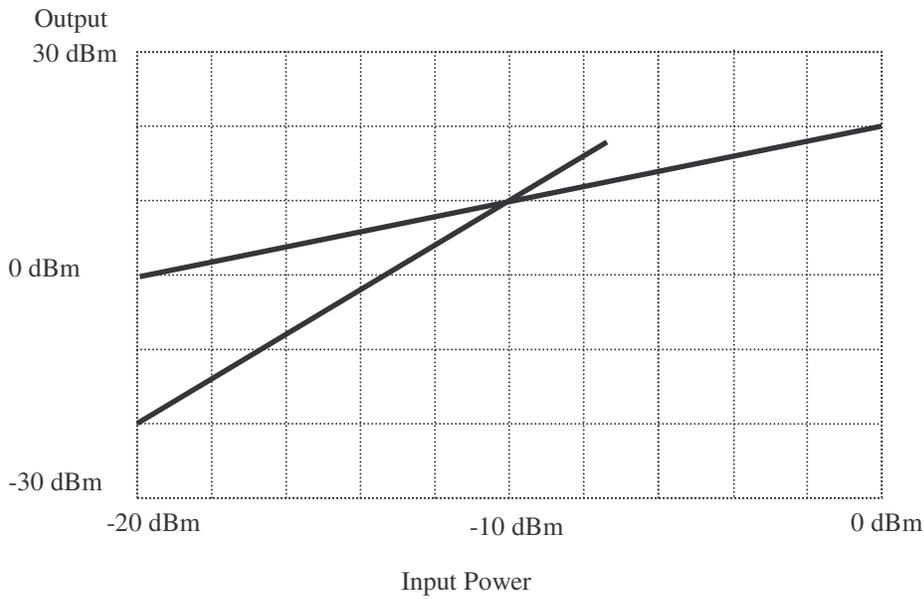- a) 1.19 nH b) 11.9 nH c) 23.8 nH d) none above

The following graph plots linear output power and third-order distortion power as a function of input power level for an amplifier.



5 Points Each

30. The gain of the amplifier is

- a) 10 dB b) 14 dB c) 20 dB d) none above

31. The output third order intercept point of the amplifier is

- a) -20 dBm b) -10 dBm c) 10 dBm d) none above

32. The input third order intercept point of the amplifier is

- a) -20 dBm b) -10 dBm c) 10 dBm d) none above